

Problem 7-17

Input Current State Next State Output

X	T2n	JK1n	JK0n	T2n...	JK1...	JK0...	A	B	C
0	0	0	0	0	1	1	0	0	0
0	0	0	1	0	1	0	0	0	1
0	0	1	0	0	1	1	0	1	0
0	0	1	1	1	0	1	0	1	1
0	1	0	0	1	1	1	1	0	0
0	1	0	1	1	1	1	1	0	1
0	1	1	0	1	0	1	1	1	0
0	1	1	1	0	0	1	1	1	1
1	0	0	0	1	1	1	0	0	0
1	0	0	1	1	1	1	0	0	1
1	0	1	0	0	0	1	0	1	0
1	0	1	1	0	1	0	0	1	1
1	1	0	0	0	1	1	1	0	0
1	1	0	1	0	1	1	1	0	1
1	1	1	0	1	0	1	1	1	0
1	1	1	1	1	0	1	1	1	1

Timing diagram, complete cycle

